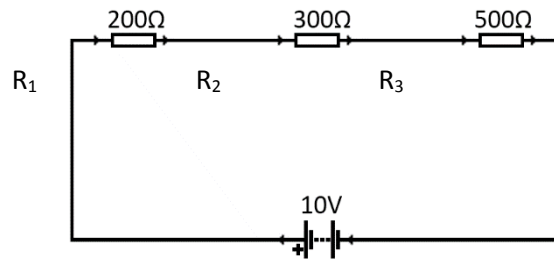


SERIES CIRCUITS.

Assembly the next series circuit:




And now, measure all the different values with the necessary measurement devices, open a spreadsheet and complete the next grid with **the values obtained.**

Device	Voltage	Current	Power =V*I
Power source			
R ₁			
R ₂			
R ₃			

ACTIVITY N°2:

PARALLEL CIRCUITS.

Assembly the next parallel circuit:

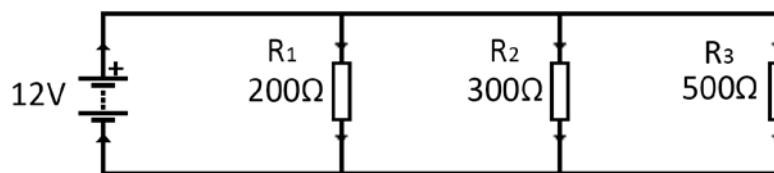


And now, measure all the different values with the necessary measurement devices, open a spreadsheet and complete the next grid with **the values obtained.**

Device	Voltage	Current	Power =V*I
Power source			
R ₁			
R ₂			
R ₃			

ACTIVITY Nº3:

MIXED CIRCUITS.

assembly the next mixed circuit:

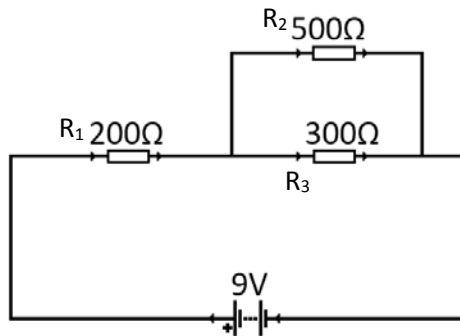

And now, measure all the different values with the necessary measurement devices, open a spreadsheet and complete the next grid with **the values obtained**.

Device	Voltage	Current	Power =V*I
Power source			
R ₁			
R ₂			
R ₃			


ACTIVITY 4 Assembly the next circuit and answer the following questions

a)

ELECTRICAL INSTALLATION 4

Being switch I closed, what will happen in the following cases?:

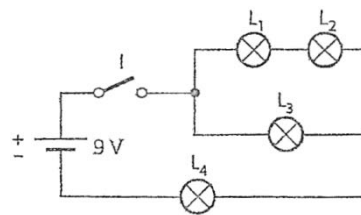- which lamp will light up more?
- which lamp will light up more if L₄ burns out?
- which lamp will light up more if L₂ burns out?
- which lamps will stop working if L₃ burns out?



ELECTRICAL INSTALLATION 5

Indicate the lamps that illuminate in the following cases:

- When switch I₃ is closed.
- When switch I₁ is closed.
- When switch I₂ is closed.
- When switches I₁ and I₂ are closed.
- When switches I₂ and I₃ are closed.
- When switches I₁ and I₃ are closed.
- When switches I₁, I₂ and I₃ are closed.

